



Instructions to Candidates:

1. All questions carry marks as indicated.
2. All the sub- questions (a, b, c, d, and e) of Que.1 in Section A are compulsory.
3. Solve any two sub-questions in Que. 2 to Que.6 in Section B.
4. Assume suitable data wherever necessary.
5. Use of non-programmable calculator is permitted.

Section A

- Que. 1. (a) Convert hexadecimal number (A0F9.0EB)₁₆ into decimal form. 2 (CO1)
- (b) Convert the Boolean expression $Y = AB + A'B'C + BC'$ into standard Boolean SOP expression. 2 (CO2)
- (c) Distinguish between combinational and sequential circuits. 2 (CO3)
- (d) Illustrate race around condition for J-K flip flop. 2 (CO4)
- (e) Write different features of 16-bit Microprocessor 8086. 2 (CO5)

Section B

- Que. 2. (a) Explain and verify De-Morgan's theorem using suitable example. 5 (CO1)
- (b) Write short notes with example: 5 (CO1)
- i) XS-3 code
- ii) Gray code
- (c) Modify following Boolean expression with reduced number of mean terms. 5 (CO1)
- i) $Y = A[B + C'(AB + AC)']$
- ii) $Y = [A + (BC)'] \cdot [(AB)' + ABC]$

- Que. 3. (a) Determine reduced SOP expression for the following and implement using logic gates, 5 (CO2)
- $$F(A, B, C, D) = \sum m(5, 6, 7, 12, 13) + d(4, 9, 14, 15)$$
- (b) Write the following Boolean expression in standard SOP and canonic form 5 (CO2)
- $$Y = A'B'D + A'B + ABC + ACD'$$

- (c) Determine reduced POS expression for the following and implement using logic gates, 5 (CO2)

$$F(A, B, C, D,) = \prod M(0,1,4,5,7, 10,11,13,14,15)$$

- Que.4 (a) Design Full adder using XOR and AOI logic gates. 5 (CO3)
- (b) Show that Full subtractor can be designed using two half subtractor. 5 (CO3)
- (c) Design 8:1 MUX using 4:1 MUX. 5 (CO3)
- Que. 5. (a) Convert the S-R flip flop into J-K flip flop. 5 (CO4)
- (b) Design and implement using JK flip flop negative edge triggered, 3-bit asynchronous up counter. 5 (CO4)
- (c) Classify different types of RAM and explain each in brief. 5 (CO4)
- Que. 6. (a) Discuss on functioning of ALU and various registers of 8085 Microprocessor. 5 (CO5)
- (b) Demonstrate different addressing modes of 8085 with one example for each. 5 (CO5)
- (c) Sketch memory read timing diagram of 8085 Microprocessor and summarize sequence of operations in it. 5 (CO5)

